

Sinking or Sourcing?

Confused about sinking and sourcing in DC circuits?

Want to find out which digital output module to use in a DC circuit?

We'll explain it here.


Let's take a quick look at the topic of sinking and sourcing outputs. How do you choose between them?

- When is it more cost-effective to choose sinking over sourcing?
- What effect does an existing electrical panel have on your choice?
- What do you do if you have a mix of sinking and sourcing wiring?

The Difference between Sinking and Sourcing

Sinking and sourcing basically refer to the two methods of wiring a digital DC circuit.


The choice is where to put the switch.

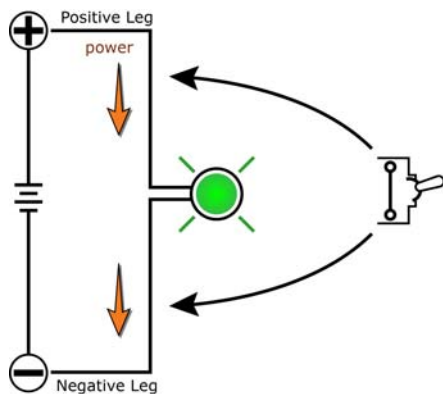

DC Circuits


In a DC circuit, power flows in one direction: from the positive side of the power source, through the load, to the negative side of the power source.

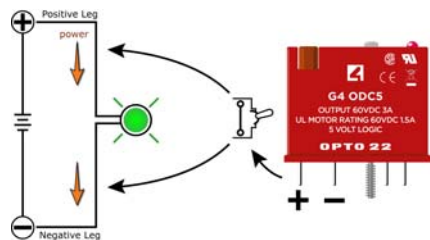To switch the load, you can place the switch either in front of the load (on the positive leg of the circuit) or behind the load, on the negative leg.




Sinking

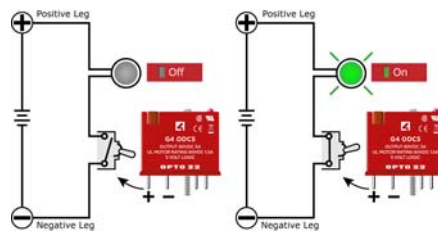Sinking is switching the load in the negative leg of the circuit, as shown below.




Sourcing

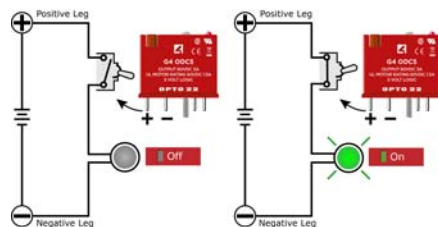Sourcing is switching the load in the positive leg of the circuit, as shown here.




Inductive Loads and Sinking

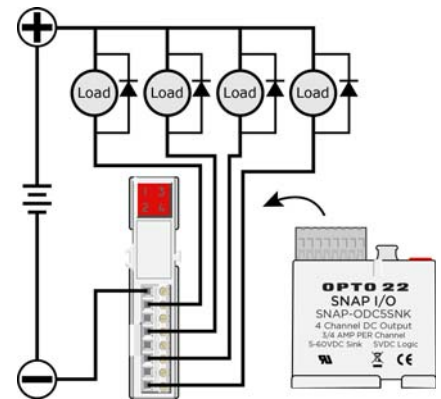When sinking inductive loads, make sure that there is a commutating diode in the circuit as shown.



Inductive Loads and Sourcing

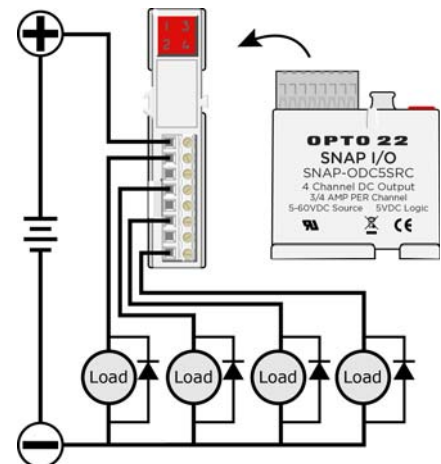When sourcing inductive loads, make sure that there is a commutating diode in the circuit as shown.




But where did the difference come from, and why would you choose one over the other?

Where does sink or source matter in automation?

Quick answer: you often have to choose a module because the device you are wiring requires either a sink or source. For example, if you have a prebuilt electrical cabinet, it may be wired using a common positive or a common negative method. Thus you HAVE to choose the correct digital output module for the way the panel is wired.

Thankfully, you don't have to worry about choosing between sinking or sourcing when it comes to alternating current. Since AC swings back and forth between a positive voltage and a negative voltage, it requires a different switching method. It's direct current (DC) where we have to choose.

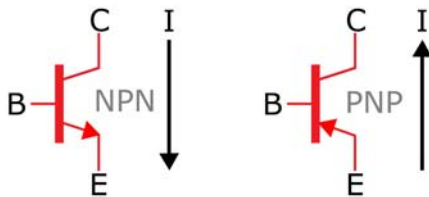A little background on the construction of transistors: there are two types, NPN and PNP. They are built differently at a silicon level and switch currents with different methods.



Back in the day (1950s to 1970s), transistors could sink (NPN) more current than they could source (PNP) for the price, so a sinking or sourcing decision made a difference in cost. In fact, even today many electronic components have asymmetric current drive ability and can switch more current to ground than to the positive rail.

The other place sinking and sourcing made a difference was on the electrical panel company's shop floor. Some companies built their panels to have a common positive rail, and some built them to have a common negative rail. Sometimes the layout of the electrical equipment lent itself to one or the other


way, but often it was simply a case of "that's how we have always done it."

This is where we, the automation guys and gals, come in to sort it all out and make it work. Since we are talking about DC circuits and how our loads are wired, we have to pick the right kind of digital output module to switch those loads.

If we are retrofitting an older non-automated control cabinet, say one that is full of relays, we need to take a look at how it's wired. We have to think about the cost of rewiring versus just buying a digital output module that will fit in with the cabinet's existing common-positive or common-negative wiring.

Sinking example, with ground as common

A modern example of this choice would be an LED quad-color stack light. (Sometimes called a tower light, it is a stack of red, yellow, green and white colored LEDs in a housing). Does it have a common positive, or a common negative? We usually cannot change the stack light wiring. It is built either way by the manufacturer. We then need to pick a digital output module that can drive the four lights to the specified rail and thus turn each of the LEDs on as required. One of the most common quad-color stack lights has a common-anode (positive) lead.

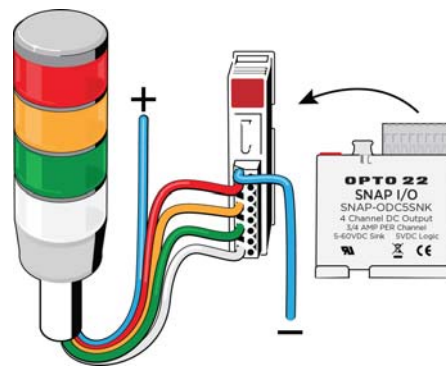

In this case we would wire that lead to the positive power supply rail, wire the other four legs to our digital output module, and then wire the digital


module's common to the negative rail of the power supply. This is a sink configuration. We turn on the digital output, the power is sourced from the positive rail, flows through the LED, is switched through the digital module, sunk to ground, and the LED is turned on. Therefore, the module you would be looking to drive this stack light would be Opto 22's [SNAP-ODCSNK](#).

To clearly see the difference between an Opto 22 sink and source module, check out our [animated demo](#).

Mixed wiring

But what if you have a mix? What if, say, your stack light is common-cathode (negative), but your machine electrical panel is wired as common-anode (positive)? Rewiring the whole panel is not an option, and neither is ordering a different stack light. You have to automate what's there. What to do?

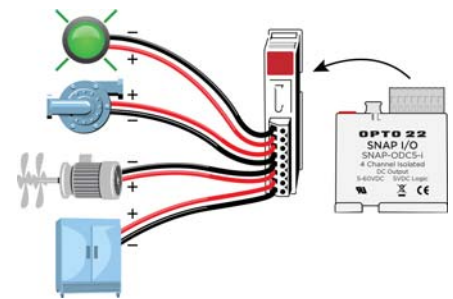In this case you can look at using an isolated module, where all 4 digital output channels are totally separate from each other. With this channel-to-channel isolation, each channel can be wired as either sinking or sourcing. In this case you could select Opto 22's [SNAP-ODCS-I](#) or [SNAP-ODCSA-I](#).



Conclusion

So there you have it. In automation we often do not have a choice. We have to choose sinking or sourcing either because of the way transistors are made, the way electrical panels are wired, or the availability of the electrical or electronic parts we are given to use.